

Week 02 : Assignment Solutions

1. Capacitive/Inductive load when connected to BJT causes abnormal switching transients during\_\_\_\_\_.

- delay time( $t_d$ )
- rise time ( $t_r$ )
- storage time ( $t_s$ )
- fall time ( $t_f$ )
- both rise time ( $t_r$ ) and fall time ( $t_f$ ).


**Ans: (e)**

Solution:

During rise time capacitive load can cause switching transient.

During fall time inductive load can cause switching transient.

2. A NPN BJT carries collector current ( $I_C$ ) of 200 mA,  $h_{FE}$  ( $\beta$ ) of the BJT is 100, base resistance ( $R_B$ ) is 500  $\Omega$  and  $V_{BE}$  is 0.6V. What is the value of  $V_{BB}$ ?

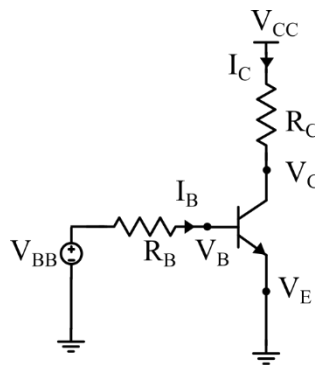

**Ans. 1.6 V [ Range: 1.4 to 1.8 ]**


Solution:

$$I_B = I_C / \beta = 2\text{mA}$$

$$V_{BB} = V_{BE} + (I_B * R_B)$$

$$= 0.6 + (2 * (10^{-3}) * 500) = 1.6 \text{ V}$$

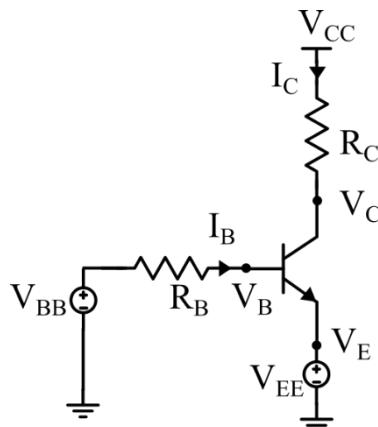3. A NPN BJT has  $h_{FE\_sat}$  ( $\beta$ ) of 100, base resistance ( $R_B$ ) is 500  $\Omega$ , load resistance ( $R_C$ ) is 30 $\Omega$ ,  $V_{BE}$  is 0.6V,  $V_{BB}$  is 5V and  $V_{CC}$  is 10V. If the BJT carries collector current ( $I_C$ ) of 200mA, what is the value of  $V_{CE}$ ?



**Ans: 0.6V [ Range: 0.55 to 0.65 ]**


**Solution:**

$$I_B = I_C / \beta = 2\text{mA}$$

$$V_{EE} = V_{BB} - (I_B \cdot R_B) - V_{BE} = 5 - (2 \cdot 10^{-3} \cdot 500) - 0.6 = 3.4\text{ V}$$

$$V_{CE} = V_{CC} - (I_C \cdot R_C) - V_{EE} = 10 - (200 \cdot 10^{-3} \cdot 30) - 3.4 = 0.6\text{V}$$

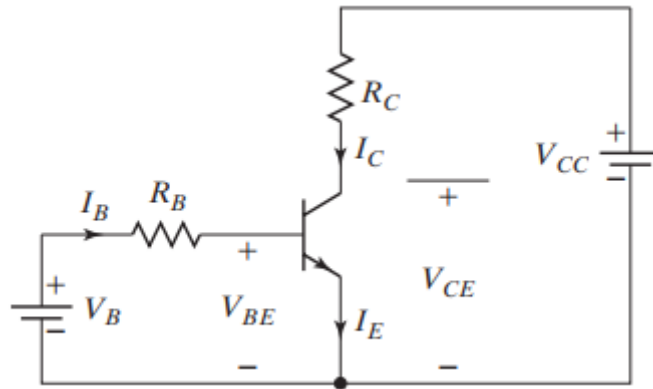- 4. In the following figure what should be the maximum value of  $R_B$  so that BJT operates in Saturation region? BJT Parameters:  $\beta$  ranges from 10 to 50;  $V_{CE(sat)} = 0.5\text{V}$ ;  $V_{BE(sat)} = 0.8\text{V}$ ;  $V_{CC} = 100.5\text{V}$ ;  $R_C = 25\text{ ohm}$ ;  $V_B = 10\text{V}$ .**



**Ans: 23 ohm [ Range: 22.9 to 23.1 ].**

**Solution:**

During the saturation region,

$$I_C = (V_{CC} - V_{CE(sat)}) / R_C = 4\text{A}$$

Min base current required to drive the BJT in saturation region,  $I_{B(sat)} \geq I_C / \beta_{min}$

$$\geq 0.4\text{A}$$

$$(V_B - V_{BE(sat)}) / R_B \geq 0.4$$

$$R_B \leq 23\text{ ohm}$$

- 5. For npn transistor which one is true:-**
- a) The base driver source ( $V_B$ ) should have sinking capability so that the negative base current can flow.
  - b) In saturation region,  $V_{CE} \geq V_{BE}$ .
  - c) The collector to emitter leakage current flows only when BJT is on.
  - d) All of the above.
  - e) A and C
  - f) A and B

**Ans: (a)**

- 6. BJT is a**
- a) Voltage controlled device
  - b) Current controlled device
  - c) Unipolar voltage device
  - d) Bipolar charge carrier device
  - e) Negative temperature coefficient device

- f) Positive temperature coefficient device
- g) All of the above
- h) None of the above

Ans: b, c, d, e

7. The gain(beta) of a npn transistor is 45. A 10 ohm resistor connected in series with collector terminal dissipates a 2.5W of power. The base current required to drive the transistor is \_\_\_\_mA.

Ans: 11.1 (Range: 10.5 to 12)

Solution:

Power dissipated by collector resistor,  $P_{loss} = I_c^2 * R_c$

Which gives,  $I_c = 0.5A$

Base Current,  $I_b = I_c / \text{gain} = 11.1mA$

8. Referring to question 7, the transistor emitter is grounded and collector resistance is connected to 15 V DC supply. The conduction loss in the transistor is \_\_\_\_W.

Ans: 5 (Range: 4.5 to 5.5)

Solution:

Drop across the  $R_c = I_c * R_c = 0.5 * 10 = 5V$ .

Collector emitter voltage,  $V_{ce} = V_{dc} - I_c * R_c = 15 - 5 = 10V$


Conduction loss,  $P_{cond} = V_{ce} * I_c = 10 * 0.5 = 5W$

9. Two identical BJT with additional resistances  $R_1$  and  $R_2$  have been connected in parallel and is supplied through a constant current source as shown in Fig. 1. Calculate the total resistance  $R_1 + R_2$  required for the following conditions:

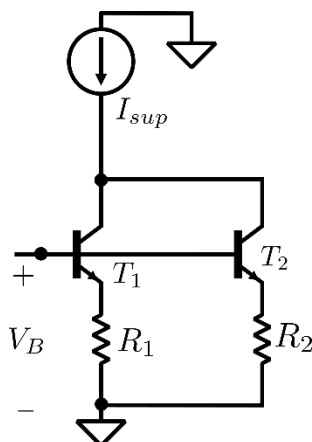1.  $V_{be1}$ (Transistor1 Base-to-emitter voltage) -  $V_{be2}$ (Transistor2 Base-to-emitter voltage) = 0.02V
2. (Current Source)  $I_{sup} = 1A$
3.  $V_B = 5V$ ;
4. For a transistor, relation between  $I_c$  and  $V_{be}$  is given by

$$I_c = I_{ss} * e^{V_{be}/nV_t}$$

where,  $I_{ss}$  = Saturation current =  $10^{(-14)}$ ,  $n=1$ ,  $V_t = 25mV$



Ans: 19.71

Solution:

$$I_{c1} = I_{ss} \cdot \exp(V_{be1}/V_t),$$

$$I_{c2} = I_{ss} \cdot \exp(V_{be2}/V_t)$$

$$I_{c1}/I_{c2} = \exp((V_{be1}-V_{be2})/V_t) \text{ ---- (1)}$$

$$I_{c1} + I_{c2} = I_{sup} \text{ ---- (2)}$$

Solving (1) and (2)

$$I_{c2} = I_{sup}/(1+\exp((V_{be1}-V_{be2})/V_t)) = 0.31A,$$

$$I_{c1} = I_{sup}-I_{c2} = 0.69A$$

$$V_{be1} = \ln(I_{c1}/I_{ss}) \cdot V_t = 0.7966V, V_{be2} = \ln(I_{c2}/I_{ss}) \cdot V_t = 0.7766V \text{ -- (ln -> log base e)}$$

$$R_1 = (V_B - V_{be1})/I_{c1} = 6.0921 \Omega, R_2 = (V_B - V_{be2})/I_{c2} = 13.6227 \Omega,$$

$$R_1+R_2 = 19.7147 \Omega$$


**10. From the above figure, If both the transistors are mounted on the same heat-sink as given below, find the thermal resistance  $R_{th\_ha}$  (heat-sink to ambient) for the condition:**

**1.  $T_{j1}$  ( $T_1$  junction temperature)=60degC,  $T_{ambient} = 25degC$**

**2.  $R_{th\_jc}$ (junction to case) =40degC/W**


**3.  $R_{th\_ch}$ (case to heat-sink) = 0.5degC/W.**

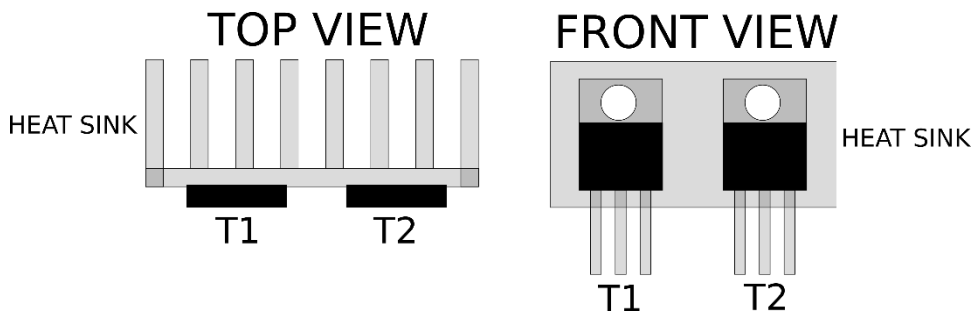**Note: Consider Heat sink temperature same throughout the heat sink body.( $V_{cesat1}=0.6V$ ,  $V_{cesat2}=0.58V$ )**



**Ans:30.7067. Range (30.65 to 30.75)**

Solution:

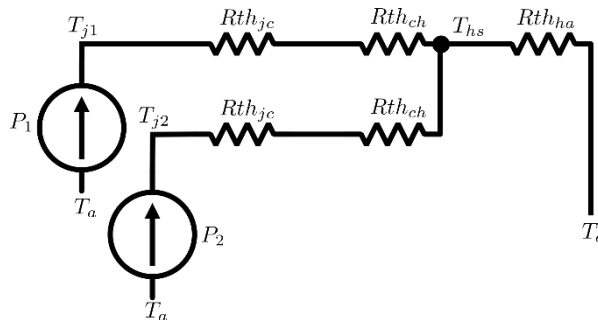

$$P_1 = V_{cesat1} \cdot I_{c1} = 0.414W,$$

$$P_2 = V_{cesat2} \cdot I_{c2} = 0.1798W$$

$$T_{j1} - T_a = P_1 \cdot (R_{th\_jc} + R_{th\_ch}) + (P_1 + P_2) \cdot R_{th\_ha}$$

$$R_{th\_ha} = ((T_{j1} - T_a) - P_1 \cdot (R_{th\_jc} + R_{th\_ch})) / (P_1 + P_2)$$

$$= ((60 - 25) - 0.414 \cdot (40.5)) / (0.5938)$$

$$= 30.7067 \text{ degC/W}$$

